

PH3204: Electronics Laboratory

Experiment 03: Study of OPerational AMPlifier (OPAMP) as inverting and non-inverting amplifier and its applications as adder and subtractor

Ronit Bhuyan (22MS025)

Sub-Group B01

March 8, 2025

Contents

1	Theory	2
2	Data and Analysis	2
3	Results and Discussion	2
4	Sources of Error	2

- 1 Theory**
- 2 Data and Analysis**
- 3 Results and Discussion**
- 4 Sources of Error**