

# PH3204: Electronics Laboratory

## Experiment 03: Study of Operational Amplifier (OpAmp) as inverting and non-inverting amplifier and its applications as adder and subtractor

Ronit Bhuyan (22MS025)

Sub-Group B01

March 11, 2025

### Contents

<b>1</b>	<b>Theory</b>	<b>2</b>
1.1	Operational Amplifier (OpAmp) . . . . .	2
1.2	Inverting Amplifier . . . . .	2
1.3	Non-Inverting Amplifier . . . . .	3
1.4	Adder . . . . .	3
1.5	Subtractor . . . . .	3
<b>2</b>	<b>Data and Analysis</b>	<b>4</b>
<b>3</b>	<b>Results and Discussion</b>	<b>4</b>
<b>4</b>	<b>Sources of Error</b>	<b>4</b>

---

# 1 Theory

## 1.1 Operational Amplifier (OpAmp)

An Operational Amplifier or OpAmp is a differential amplifier that has a very high voltage gain, high input impedance and low output impedance. The OpAmp has two inputs namely a non-inverting input ( $V_+$ ) and an inverting input ( $V_-$ ). The OpAmp amplifies the difference between the two inputs. The output voltage ( $V_{out}$ ) is given by

$$V_{out} = A(V_+ - V_-)$$

where  $A$  is the open loop gain of the amplifier. The OpAmp is usually operated with a negative feedback. The OpAmp used in this experiment is the LM741 OpAmp. The pin configuration of the LM741 OpAmp and its circuit diagram is shown in the figure below.

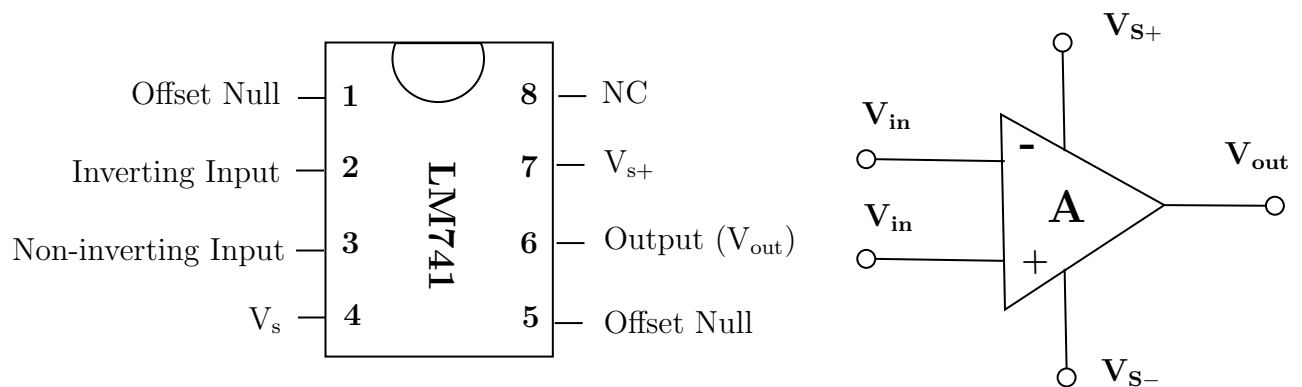


Figure 1: Pin configuration of LM741 OPAMP (left) and its circuit symbol (right)

The OpAmp can be used in various configurations such as inverting amplifier, non-inverting amplifier, adder, subtractor, differentiator, integrator etc. In this experiment, we will study the OpAmp as an inverting amplifier, non-inverting amplifier, adder and subtractor.

## 1.2 Inverting Amplifier

The OpAmp can be used as an inverting amplifier by connecting it as per the following circuit diagram.

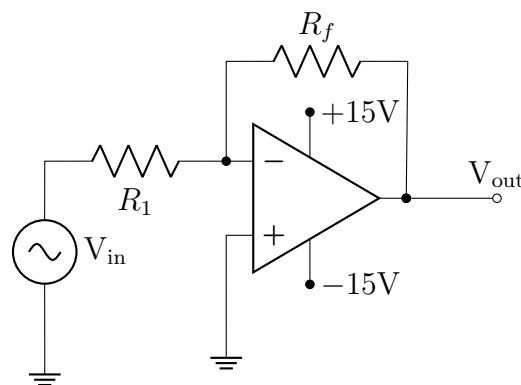


Figure 2: Circuit diagram of OpAmp as an Inverting Amplifier

### 1.3 Non-Inverting Amplifier

The circuit diagram of an OpAmp as a non-inverting amplifier is shown below.

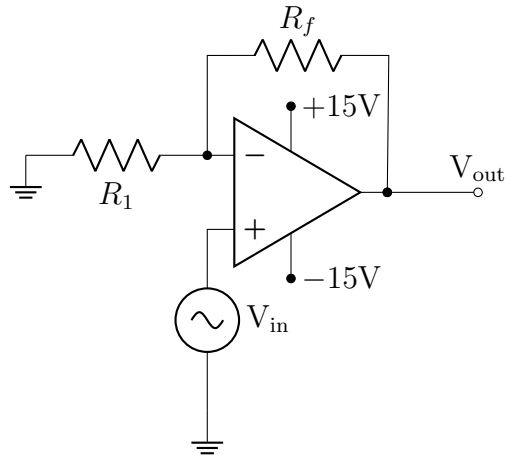


Figure 3: Circuit diagram of OpAmp as a Non-Inverting Amplifier

### 1.4 Adder

The OpAmp can be used as an adder by connecting it as per the following circuit diagram.

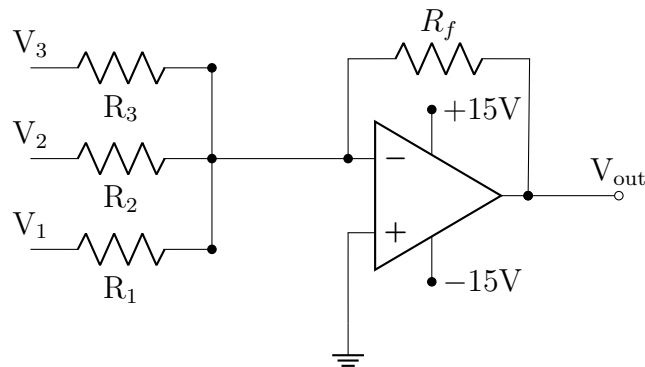


Figure 4: Circuit diagram of OpAmp as an Adder

### 1.5 Subtractor

The circuit diagram for OpAmp as a subtractor is shown below.

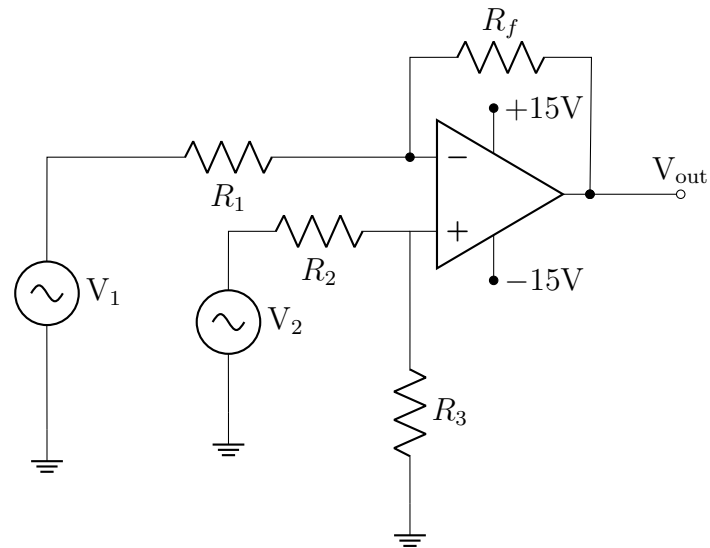


Figure 5: Circuit diagram of OpAmp as a Subtractor

**2 Data and Analysis**

**3 Results and Discussion**

**4 Sources of Error**