

PH3204: Electronics Laboratory

Experiment 04: Study of Boolean algebra truth tables for Logic Gate functions using AND, OR, NAND, NOR etc. ICs

Ronit Bhuyan (22MS025)

Sub-Group B01

March 31, 2025

Contents

1	Theory	2
2	Boolean Circuit Verification	3
2.1	Example 1	4
2.2	Example 2	5
2.3	Example 3	6
3	Conclusion	7
4	Sources of Error	7

1 Theory

Boolean algebra deals with variables only two possible output, 0 and 1 (false and true). A Boolean function takes in one or more boolean inputs and produces a boolean output. A boolean function can be implemented in the form of a boolean circuit using logic gates. Some of the most common logic gates along with their truth tables are given below:

- NOT Gate

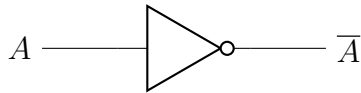


Figure 1: Symbol of NOT Gate

A	\overline{A}
0	1
1	0

Table 1: Truth Table for NOT Gate

- AND Gate

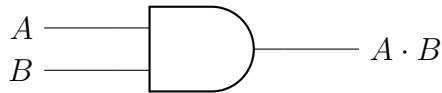


Figure 2: Symbol of AND Gate

A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Table 2: Truth Table for AND Gate

- OR Gate

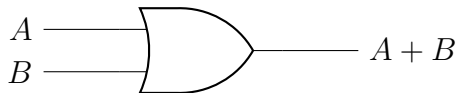


Figure 3: Symbol of OR Gate

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Table 3: Truth Table for OR Gate

- NAND Gate

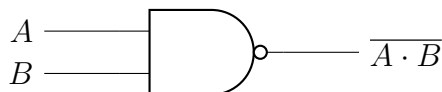


Figure 4: Symbol of NAND Gate

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Table 4: Truth Table for NAND Gate

- **NOR Gate**

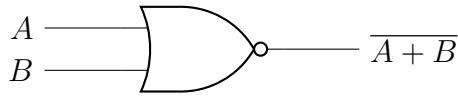


Figure 5: Symbol of NOR Gate

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Table 5: Truth Table for NOR Gate

- **XOR Gate**

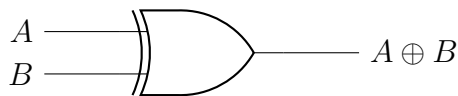


Figure 6: Symbol of XOR Gate

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Table 6: Truth Table for XOR Gate

In our experiment, we have used ICs for implementing the above mentioned logic gates. The ICs used are listed below:

- **IC7400:** NAND Gate
- **IC7402:** NOR Gate
- **IC7404:** NOT Gate
- **IC7408:** AND Gate
- **IC7432:** OR Gate
- **IC7486:** XOR Gate

2 Boolean Circuit Verification

We shall verify three different boolean circuits in this experiment. The circuits are drawn with using ICs, bread boards and the output is observed using an LED Bulb. The glowing of the LED indicates an output 1 while 0 is indicated by the LED not glowing.

2.1 Example 1

In each of the cases , we observed that the experimental output of the circuit matched with what was expected from the theoretical expression. The truth table for the circuit was hence verified to be correct.

2.2 Example 2

The second boolean circuit that we shall verify is given below:

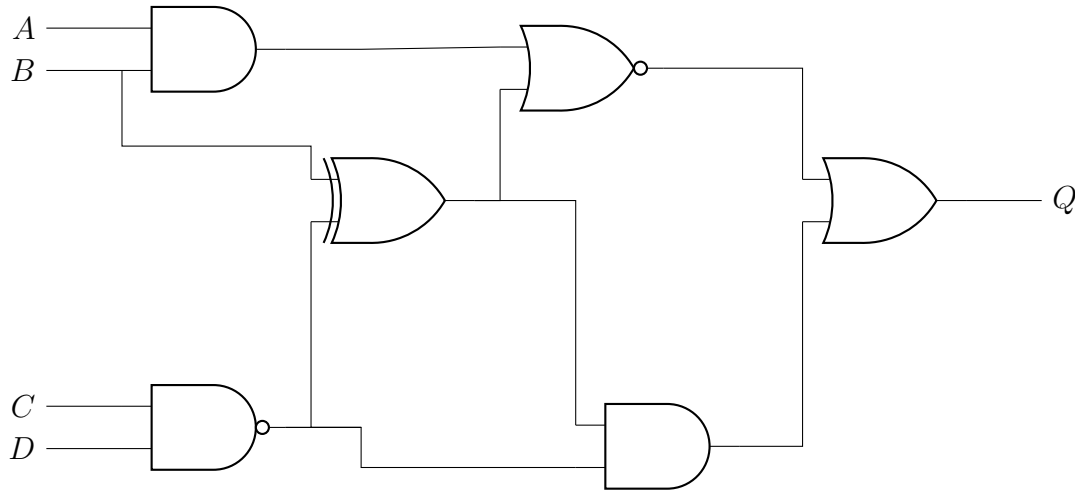


Figure 8: Boolean Circuit for Example 2

The theoretical boolean expression of the circuit is given by:

$$Q = \overline{A} \cdot (\overline{C} \cdot \overline{D}) + \overline{B}$$

Experimentally, the truth table for the circuit drawn above has been tabulated below:

A	B	C	D	Q
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0

A	B	C	D	Q
1	1	1	0	0
1	1	1	1	0

Table 8: Truth Table for Example 2

In each of the cases, we observed that the experimental output of the circuit matched with what was expected from the theoretical expression. The truth table for the circuit was hence verified to be correct.

2.3 Example 3

The final example that we shall verify is shown below:

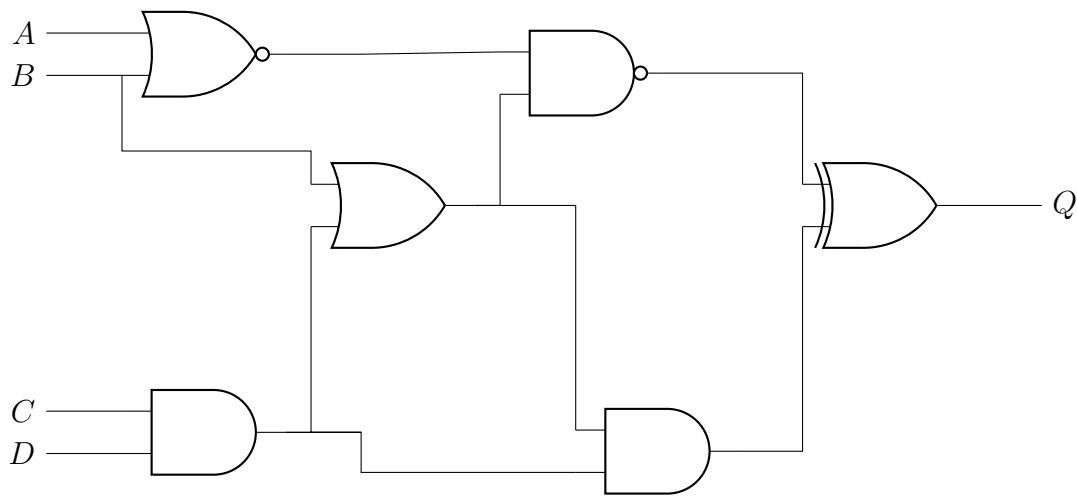


Figure 9: Boolean Circuit for Example 3

$$Q = \overline{A}.\overline{B} + \overline{C} + \overline{D}$$

Experimentally, the truth table for the circuit drawn above has been tabulated below:

A	B	C	D	Q
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1

A	B	C	D	Q
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Table 9: Truth Table for Example 3

In each of the cases , we observed that the experimental output of the circuit matched with what was expected from the theoretical expression. The truth table for this circuit was hence verified to be correct as well.

3 Conclusion

In this experiment, we studied three different boolean circuits made from a combination of different logic gates and verified the truth tables for each of the circuit. In each case , the truth tables were verified to be correct.

4 Sources of Error

The following sources of error were observed during the experiment:

- The connections made on the bread board may not very stable and hence could give rise to incorrect results. Errors may also occur due to disfunctioning of the ICs used.
- The LED Bulb used to indicate the output maybe not be bright enough. This could cause difficulty and errors in observing the output.